

Two Port Networks


By

P V S R Bharadwaja


Introduction

- A Pair of terminals through which a current may enter or leave a network is known as a port.
- A port is an access to the network and consists of a pair of terminals; the current entering one terminal leaves through the other terminal so that the net current entering the port equals zero.
- A two-port network is an electrical network with two separate ports for input and output.

Network With One Port

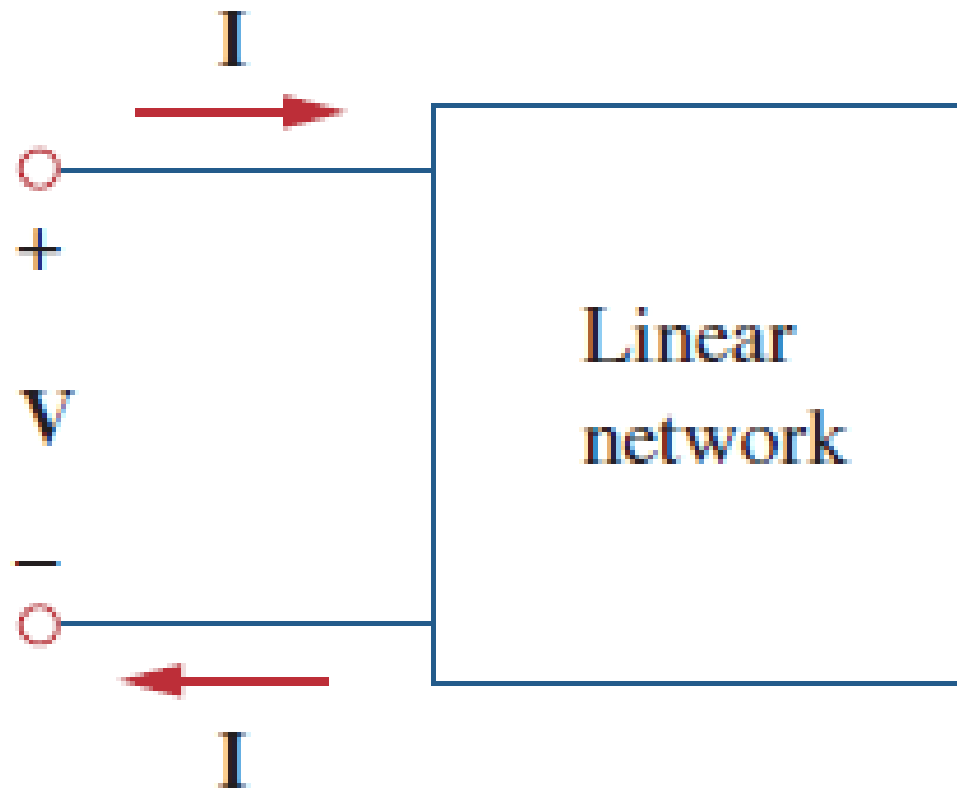

Two Port Networks

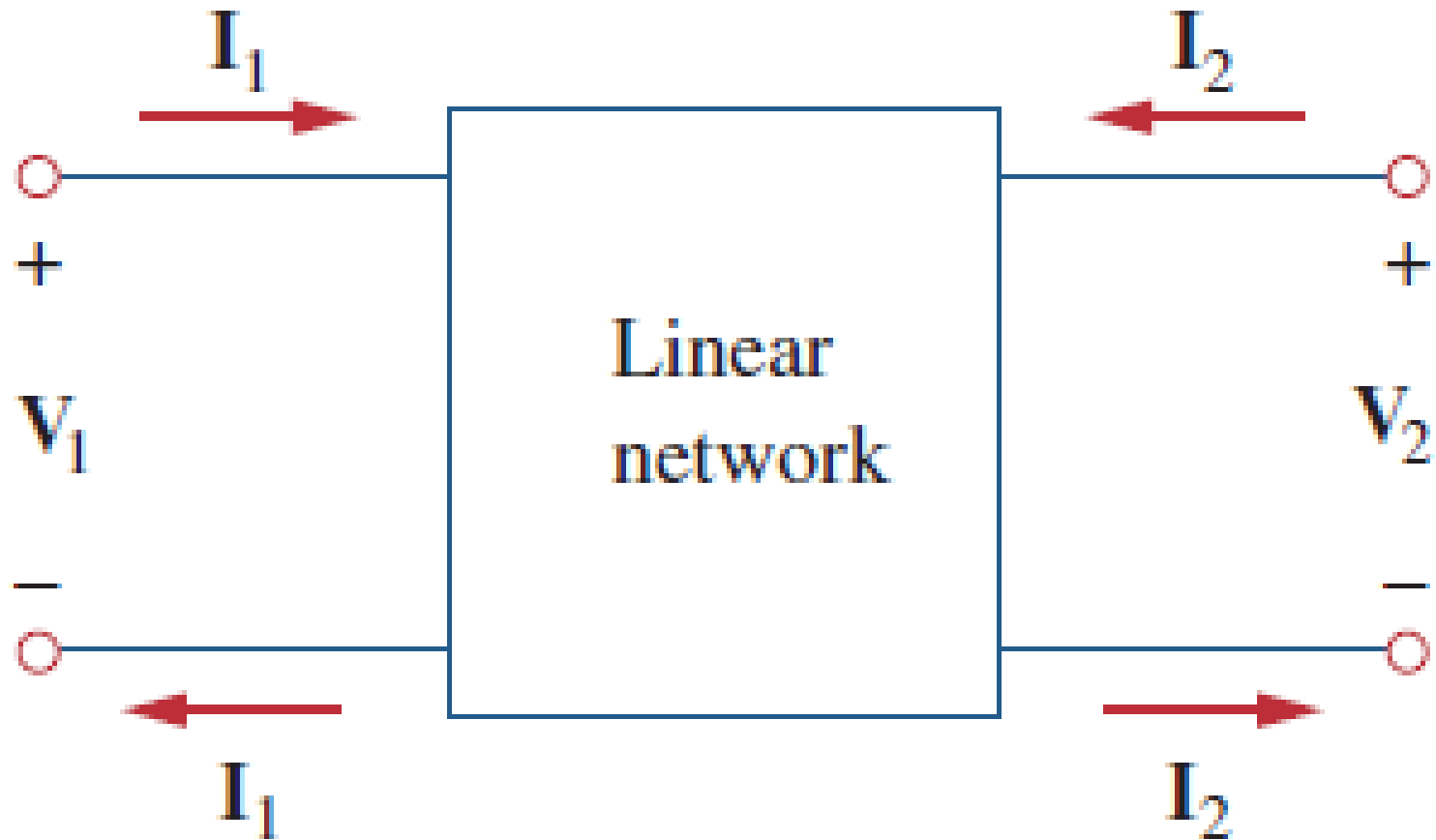

Reasons for Studying Two Port Networks

- They are useful in Communications, Electronics, Control Systems Etc
 - Ex: They are used in modelling transistors in transistors
- Knowing the parameters of a two port network enables us to treat it as a “Black Box” when embedded within a larger network

List of Two Port Parameters

- Impedance Parameters
 - Admittance Parameters
 - Hybrid Parameters
 - Transmission Parameters
-
- * Interconnection of Parameters
 - * Conditions of Reciprocity and Symmetry

1. Impedance Parameters


- They are commonly used in Synthesis of Filters
- They are useful in Design and Analysis of Impedance Matching Networks and Power Distribution networks
- In all the networks only two variables will be independent and remaining two will be dependent

$$\mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$

$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2$$

Z Parameters in the form of Matrix
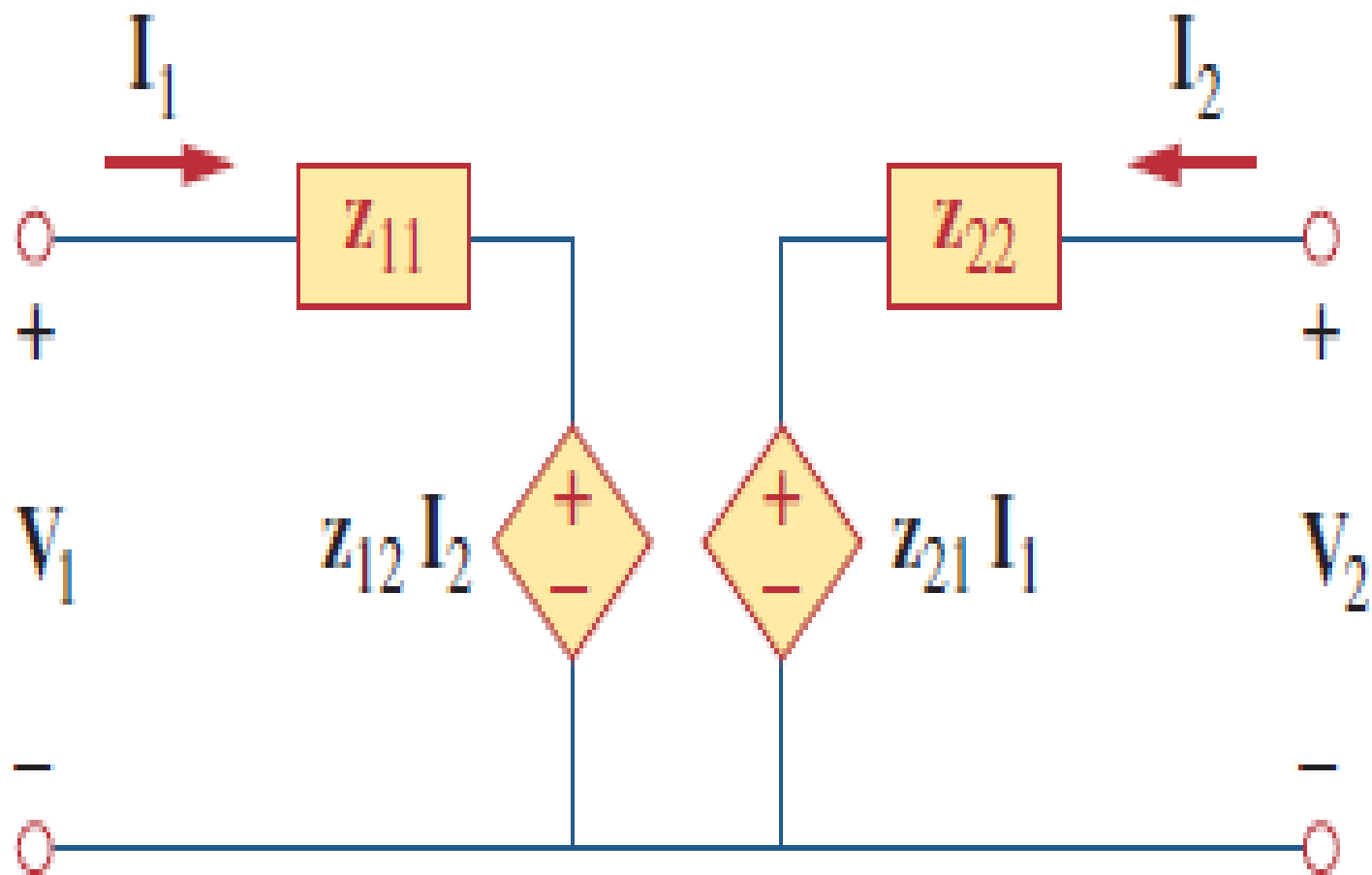
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [z] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



Z Parameters Relationship

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}, \quad Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}, \quad Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

Name of Z Parameters

z_{11} = Open-circuit input impedance

z_{12} = Open-circuit transfer impedance from port 1 to port 2

z_{21} = Open-circuit transfer impedance from port 2 to port 1

z_{22} = Open-circuit output impedance

Driving Point Impedance


- A driving point impedance is the input impedance of a two terminal device.
- Z_{11} : Input Driving Point Impedance with Output open circuited
- Z_{22} : Output Driving Point Impedance with Input Open Circuited

Transfer Impedances

- Z_{21} and Z_{22} are called Transfer Impedances


Graphical Approach - I

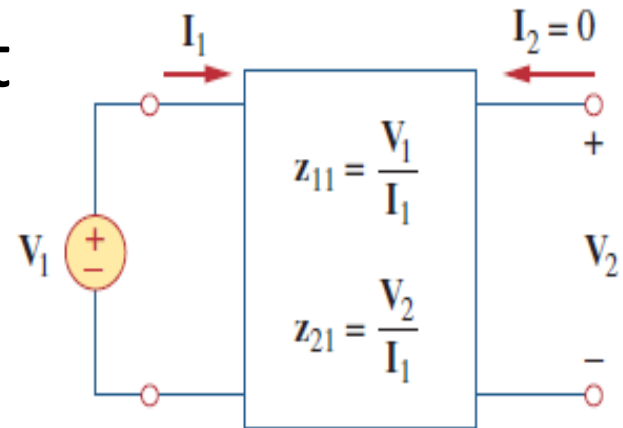- Step 1 : Connect V_1 to port 1
- Step 2 : Apply KVL at input Loop
- Step 3 : Find Z_{11} and Z_{21}



Graphical Approach - II

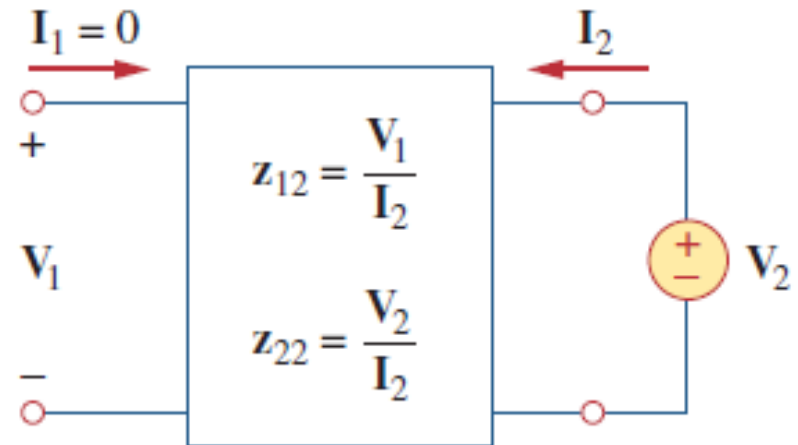- Step 1 : Connect V_2 to Port 2
- Step 2 : Apply KVL to Output Loop
- Step 3 : Find Z_{12} and Z_{22} .




Whether Symmetrical ?

When $z_{11} = z_{22}$, the two-port network is said to be *symmetrical*. This implies that the network has mirrorlike symmetry about some center line; that is, a line can be found that divides the network into two similar halves.


Whether Reciprocal ?

- When the two-port network is linear and has no dependent sources, the transfer impedances are equal ($Z_{12} = Z_{21}$) and the two port is said to be *reciprocal*.

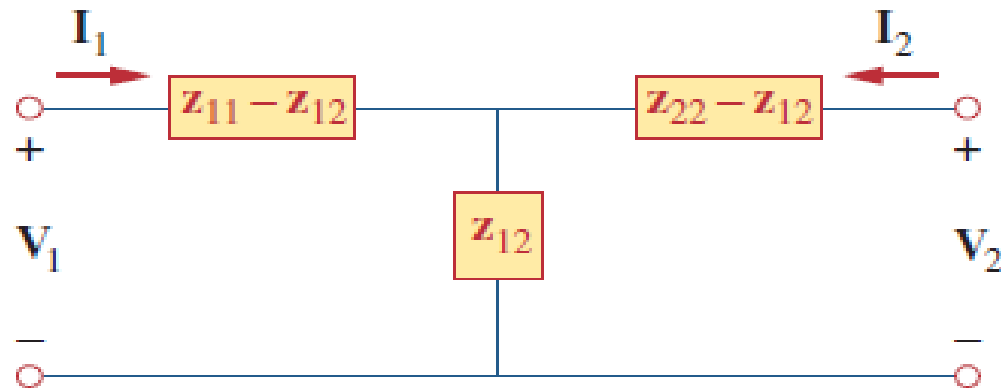


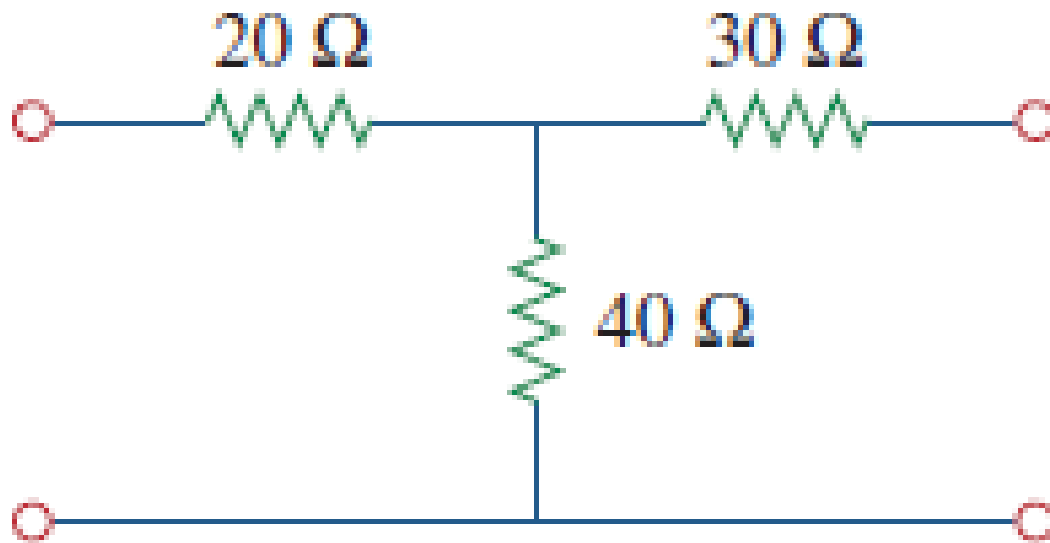Problem 1

- Determine the Z- Parameters for the below circuit



Circuit 1 for Calculation of Parameters

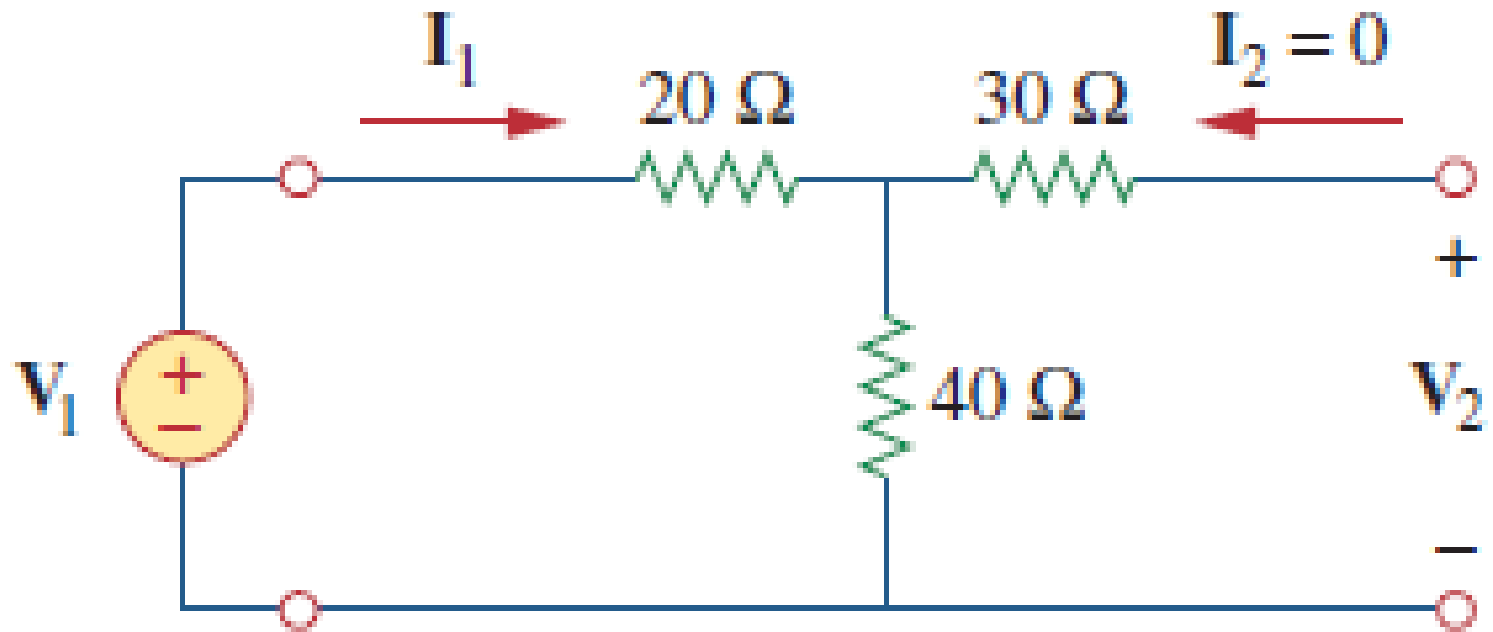


Calculation of Z_{11} and Z_{21}

$$Z_{11} = \frac{V_1}{I_1} = \frac{(20 + 40)I_1}{I_1} = 60 \, \Omega$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{40I_1}{I_1} = 40 \, \Omega$$

Circuit 2 For Calculation of Parameters

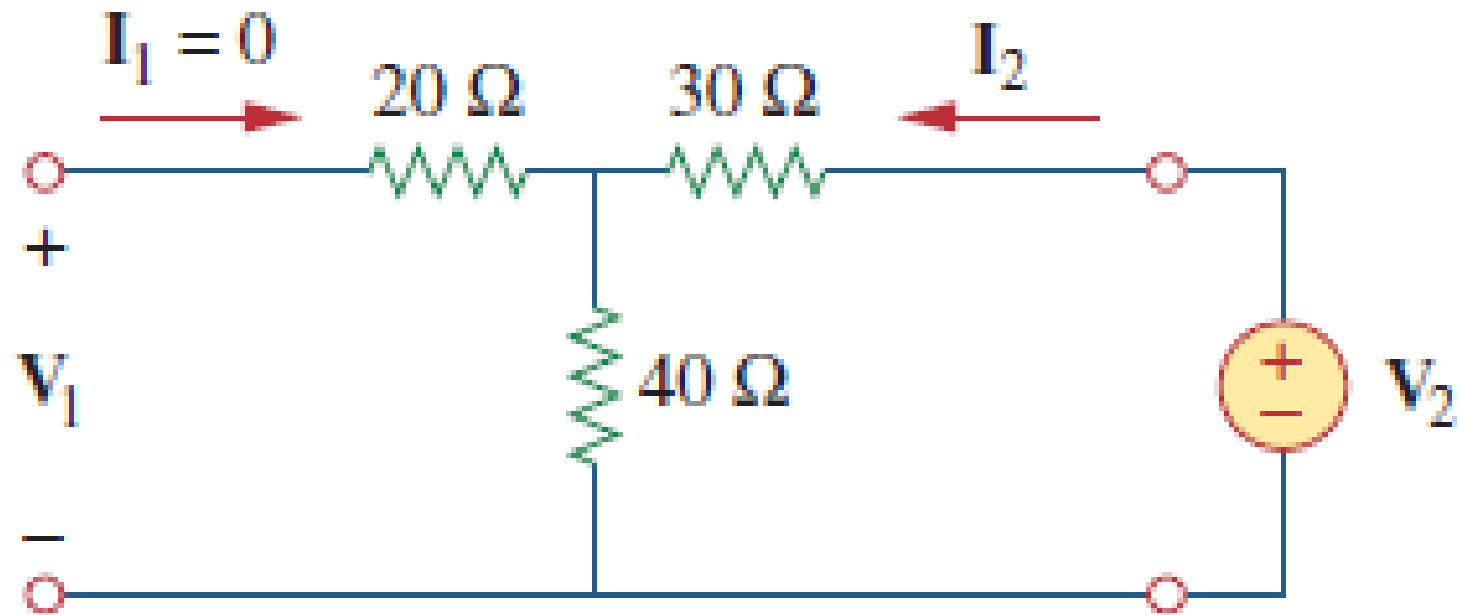

Calculation of Z_{12} and Z_{22}

$$Z_{12} = \frac{V_1}{I_2} = \frac{40I_2}{I_2} = 40 \, \Omega,$$


$$Z_{22} = \frac{V_2}{I_2} = \frac{(30 + 40)I_2}{I_2} = 70 \, \Omega$$

Impedance Matrix

$$[Z] = \begin{bmatrix} 60 \, \Omega & 40 \, \Omega \\ 40 \, \Omega & 70 \, \Omega \end{bmatrix}$$

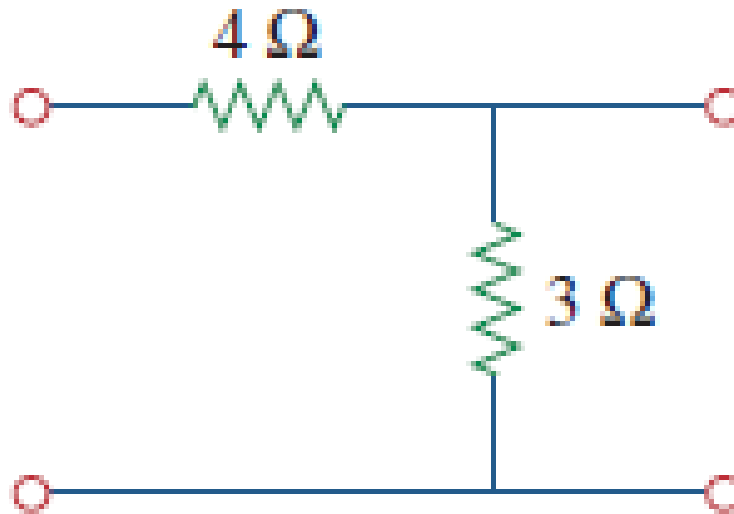Problem 2


- Find the Z- Parameters for the Below Network



Answer: $z_{11} = 7\ \Omega, z_{12} = z_{21} = z_{22} = 3\ \Omega.$

Problem 3

- Find I_1 and I_2

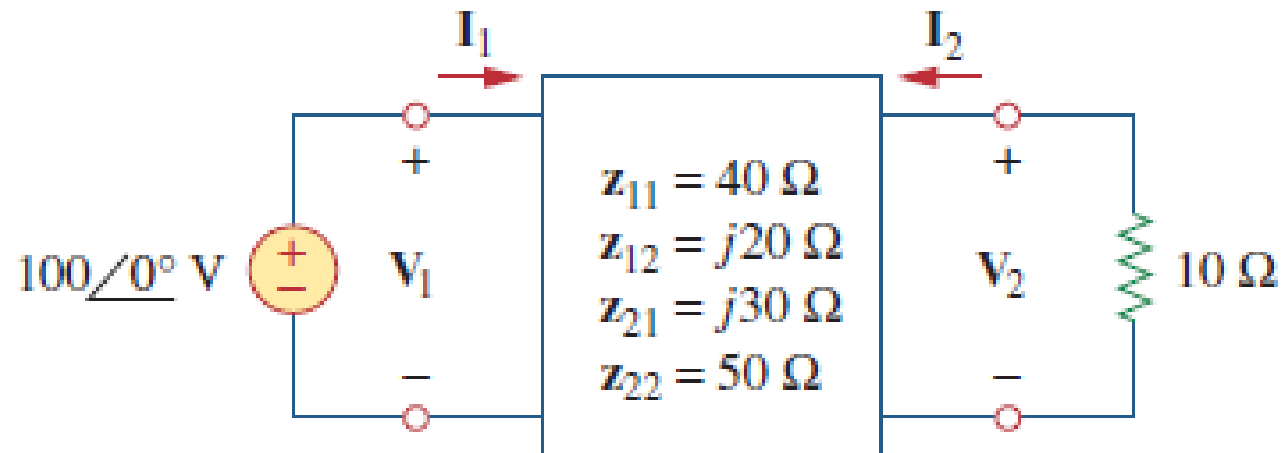

$$\mathbf{I_1 = 2 \angle 0^\circ A, \quad I_2 = 1 \angle -90^\circ A}$$

Problem 4

- Find the Z-Parameters for the below circuit

